

Department of Physics  
Periyar Arts College, Cuddalore

III B.Sc . PHYSICS

Elective - Digital Electronics

6-8-2020 10 AM- 11AM

UNIT 5

Introduction to D/A and A/D  
Converters

**Binary Weighted Resistor DAC**


Slides prepared by JA

# ANALOG SIGNALS


(Continuously Changing with time)

- Pressure Variations
- Light Intensity Variations
- Sound Signal
- Video Signal
- ECG Signals
- Temperature Variations
- Any Physical Quantity from transducers
- The real world deals with only Analog signals
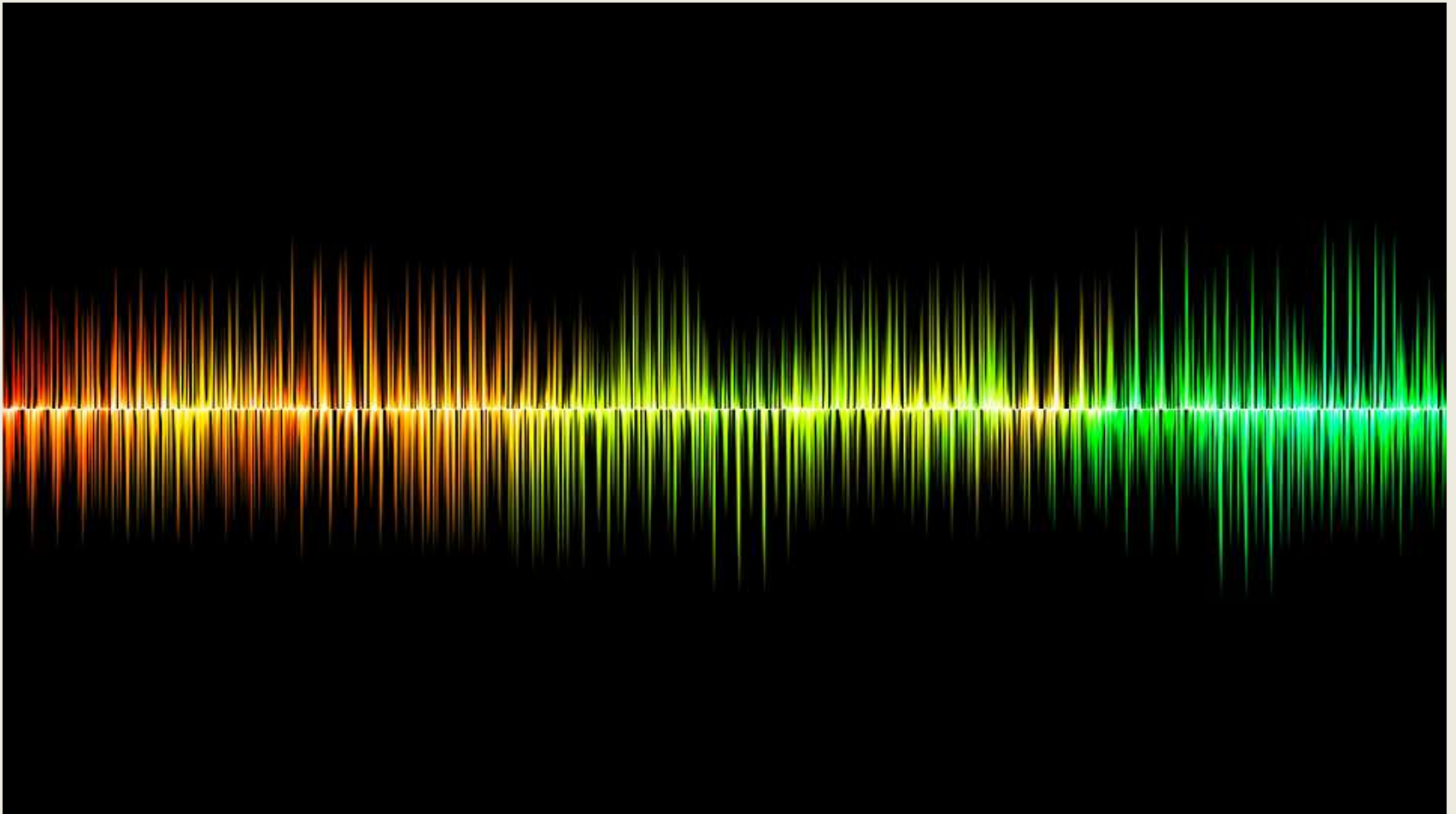
# Voice Signal from Microphone (Analog Signal)


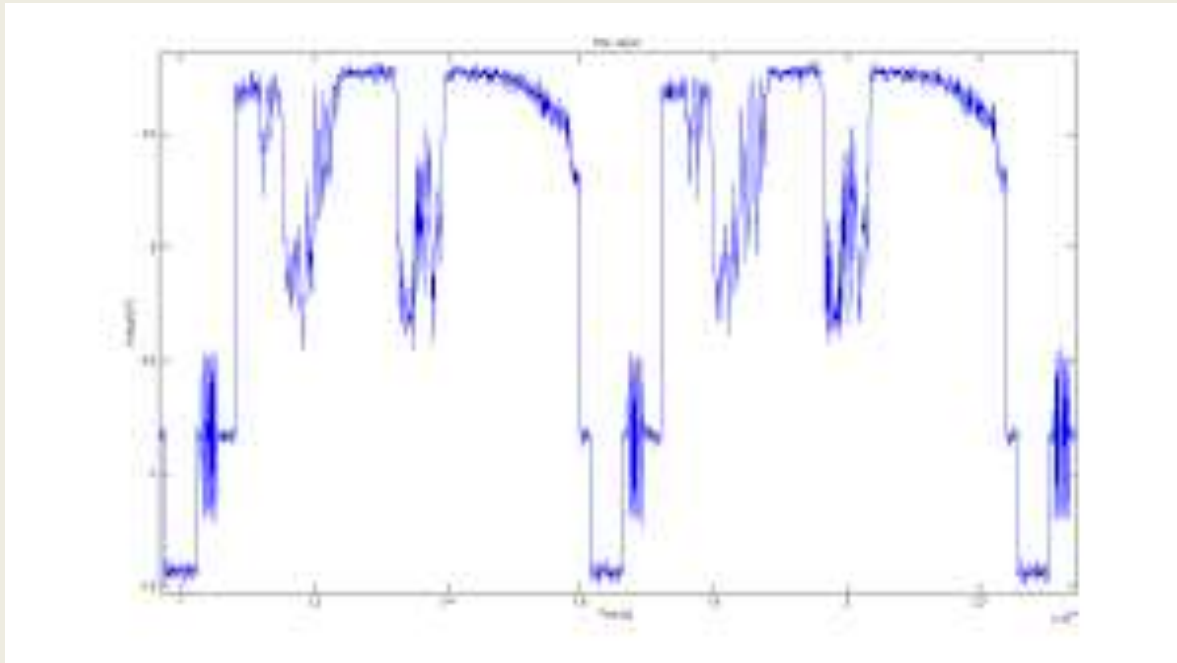
# Composite Video Signal (TV) (Analog Signal)



# ECG Signal (Analog signal)

## Electro Cardio Graph



### Human Heart beat pulses


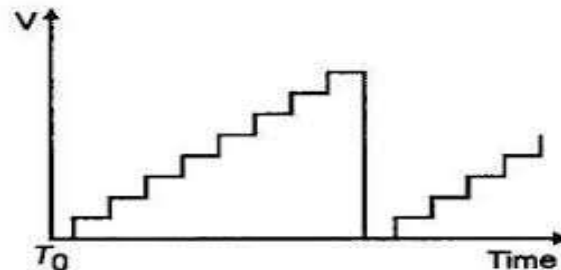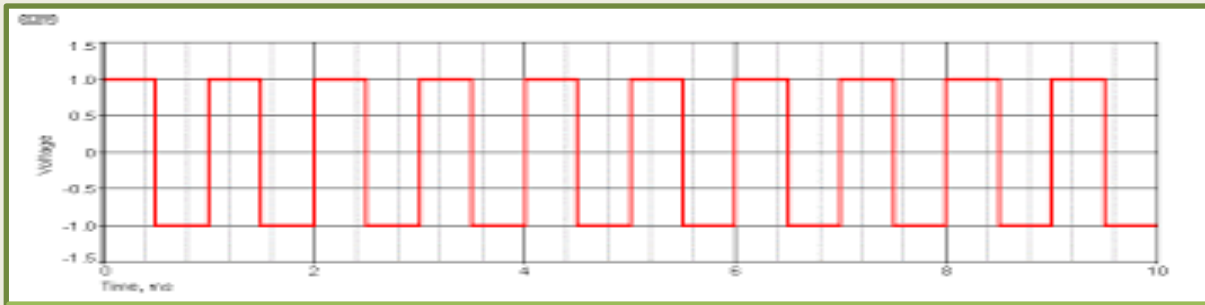
# DIGITAL SIGNALS


(Discrete signals, 0 or 1)

Computer Data (Square, Rectangular pulses, Clock Pulses, Staircase waveforms)





- A digital to analog converter (DAC) converts a digital signal to an analog voltage or current output.


100101...

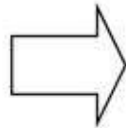

DAC

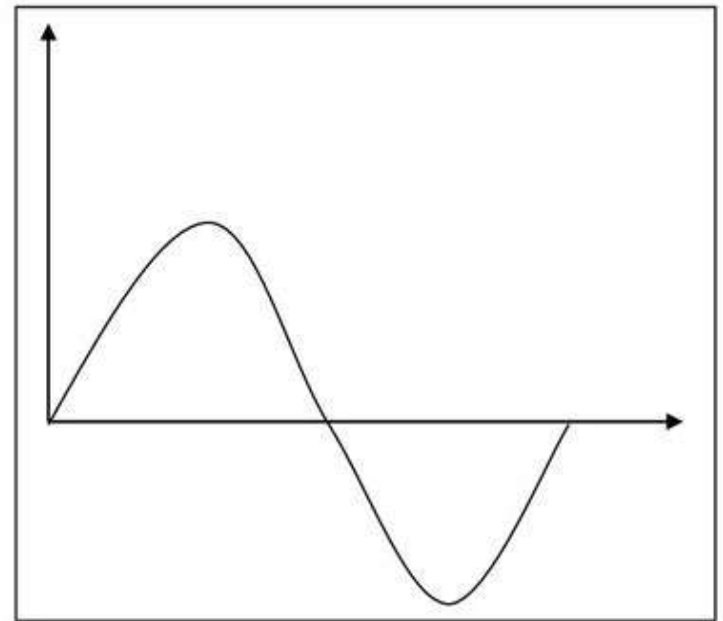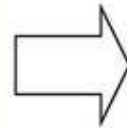



# CONVERSION A/D and D/A

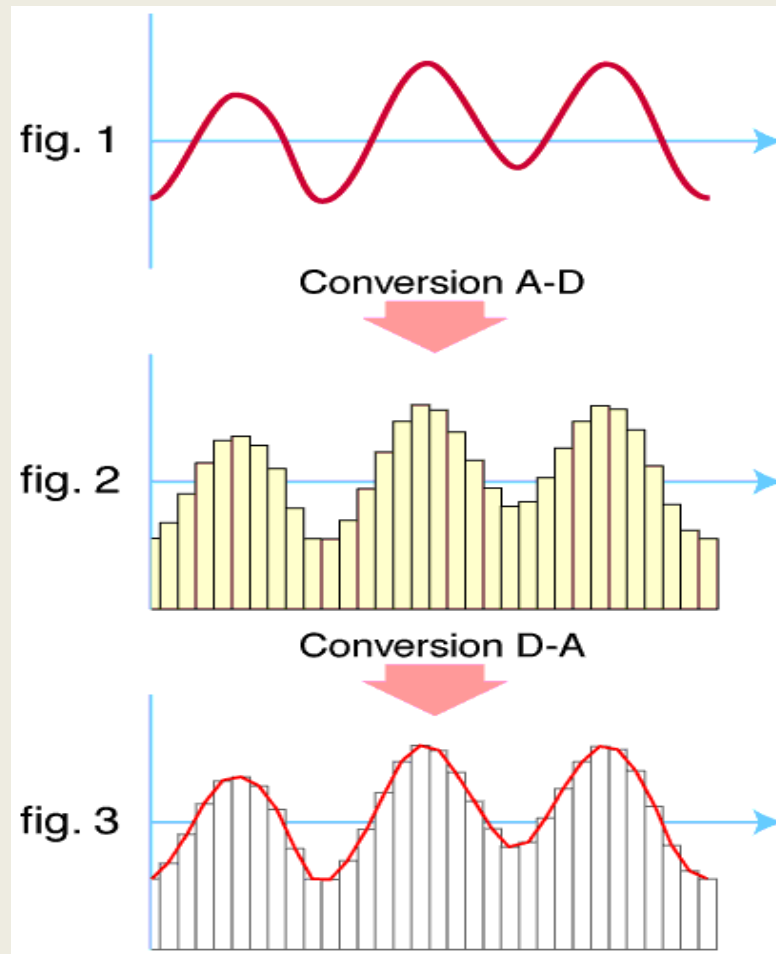



# NEED FOR CONVERSION

## Need of conversion

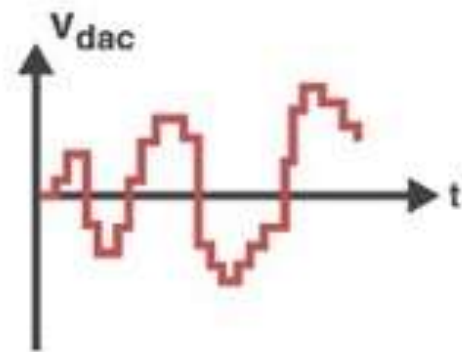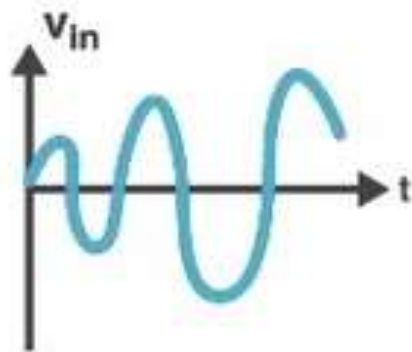

# Binary Weighted Resistor DAC (4 bits)

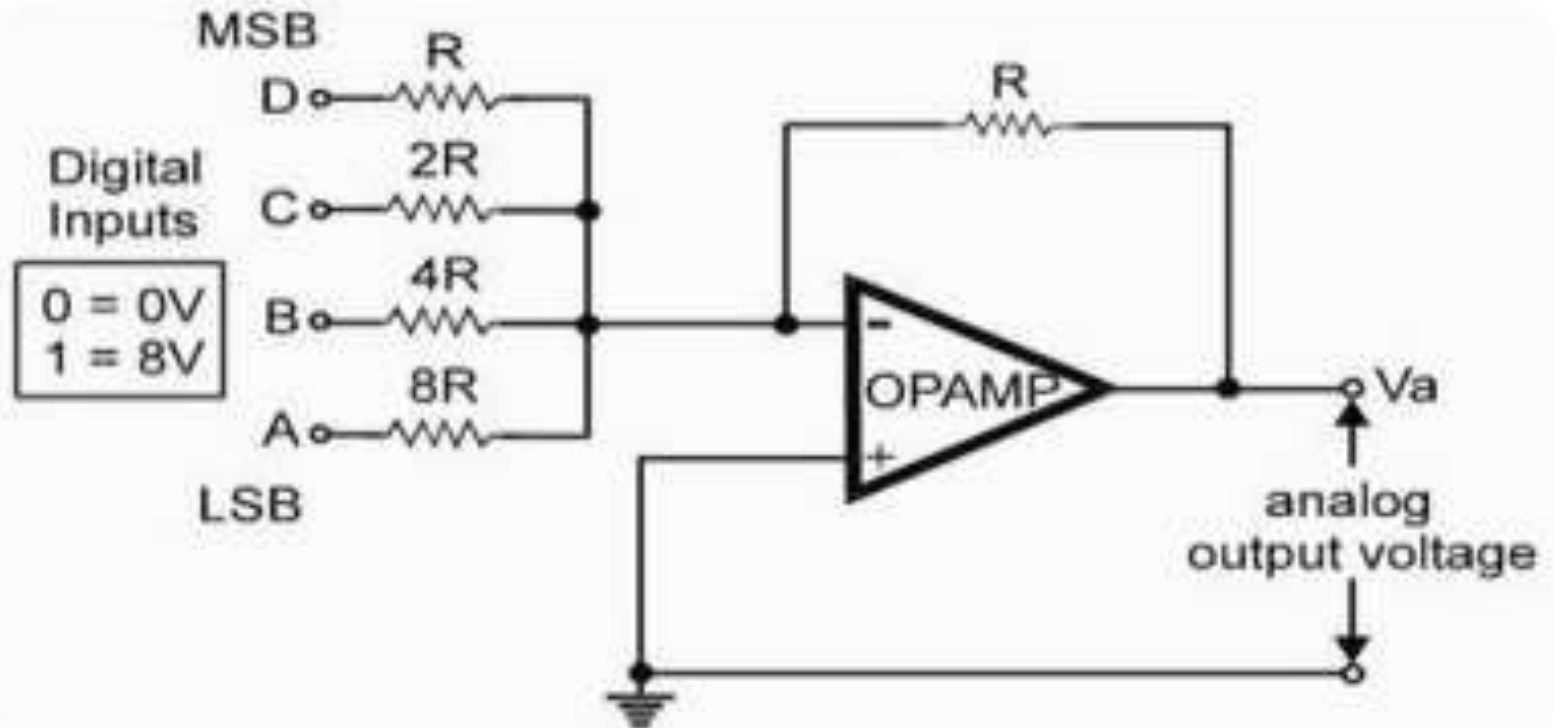


Figure: Weighted resistors D/A converter

# WORKING of 4 Bit DAC

Currents flowing through Input Resistances, **R**, **2R**, **4R**, **8R**, as the **inverting input** of op-amp acts as **Virtual ground**,

$$1) \quad I_D = \frac{V_{ref}}{R}$$

$$2) \quad I_C = \frac{V_{ref}}{2R}$$

$$3) \quad I_B = \frac{V_{ref}}{4R}$$

$$4) \quad I_A = \frac{V_{ref}}{8R}$$

Total current flowing through the feedback resistor R,

$$I = I_D + I_C + I_B + I_A$$

Output voltage,  $V_o = - I R$

Therefore,  $V_o = - (I_D + I_C + I_B + I_A) R$

Since the circuit is **summing amplifier**, its **output** is given by the following equation

$$V_0 = -R \left( \frac{D}{R} + \frac{C}{2R} + \frac{B}{4R} + \frac{A}{8R} \right) V_{\text{ref}}$$

Here  $V_{\text{ref}} = 8 \text{ Volts}$

**D, C, B, A** are digital inputs, either 0 or 1

# Output Voltage Calculations

- D is the MSB,  
Most Significant Bit
- A is the LSB,  
Least Significant Bit

## Case i

When input **DCBA = 0000**, and  
 **$V_{\text{ref}} = 8$  Volts**

then

$$V_0 = -R \left( \frac{0}{R} + \frac{0}{2R} + \frac{0}{4R} + \frac{0}{8R} \right) 8$$

$$V_0 = 0 \text{ Volts}$$

# Output Voltage Calculations

## Case ii

When digital input of the circuit DCBA = 0001,

$$V_0 = -R \left( \frac{0}{R} + \frac{0}{2R} + \frac{0}{4R} + \frac{1}{8R} \right) 8$$

$$V_0 = -R \left( \frac{8}{8R} \right) = -1 V$$

## Case iii

When digital input of the circuit DCBA = 0010

$$V_0 = -R \left( \frac{0}{R} + \frac{0}{2R} + \frac{1}{4R} + \frac{0}{8R} \right) 8$$

$$V_0 = -R \left( \frac{8}{4R} \right) = -2 \text{ Volts}$$

And so on....


In this way, when digital input **DCBA** changes from **0000** to **1111** (in BCD style), output voltage ( $V_o$ ) changes proportionally.

$$V_{\text{ref}} = 8 \text{ volts}$$

D	C	B	A	$V_o$ (volts)
0	0	0	0	0
0	0	0	1	-1
0	0	1	0	-2
0	0	1	1	-3
0	1	0	0	-4
0	1	0	1	-5
0	1	1	0	-6
0	1	1	1	-7
1	0	0	0	-8
1	0	0	1	-9
1	0	1	0	-10
1	0	1	1	-11
1	1	0	0	-12
1	1	0	1	-13
1	1	1	0	-14
1	1	1	1	-15




# DAC Output Waveform

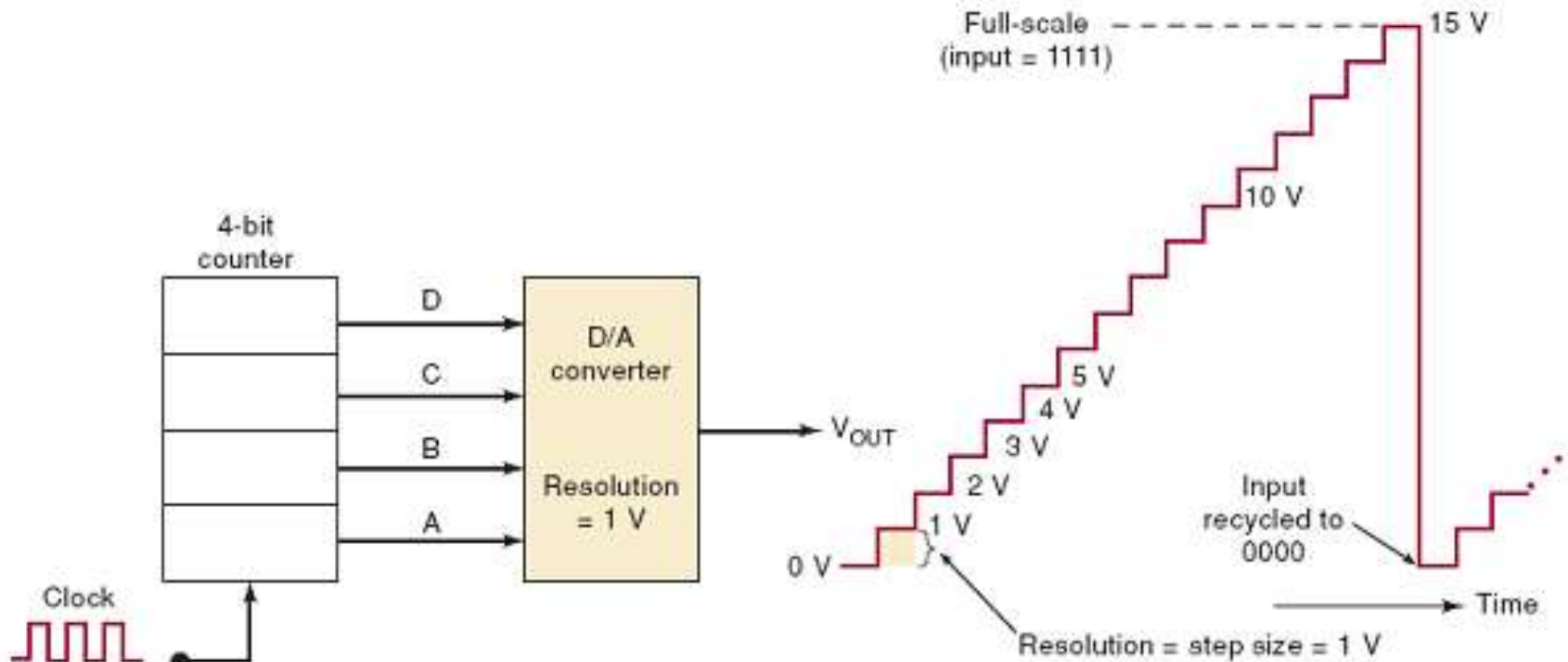

**FIGURE 11-3** Output waveforms of a DAC as inputs are provided by a binary counter.
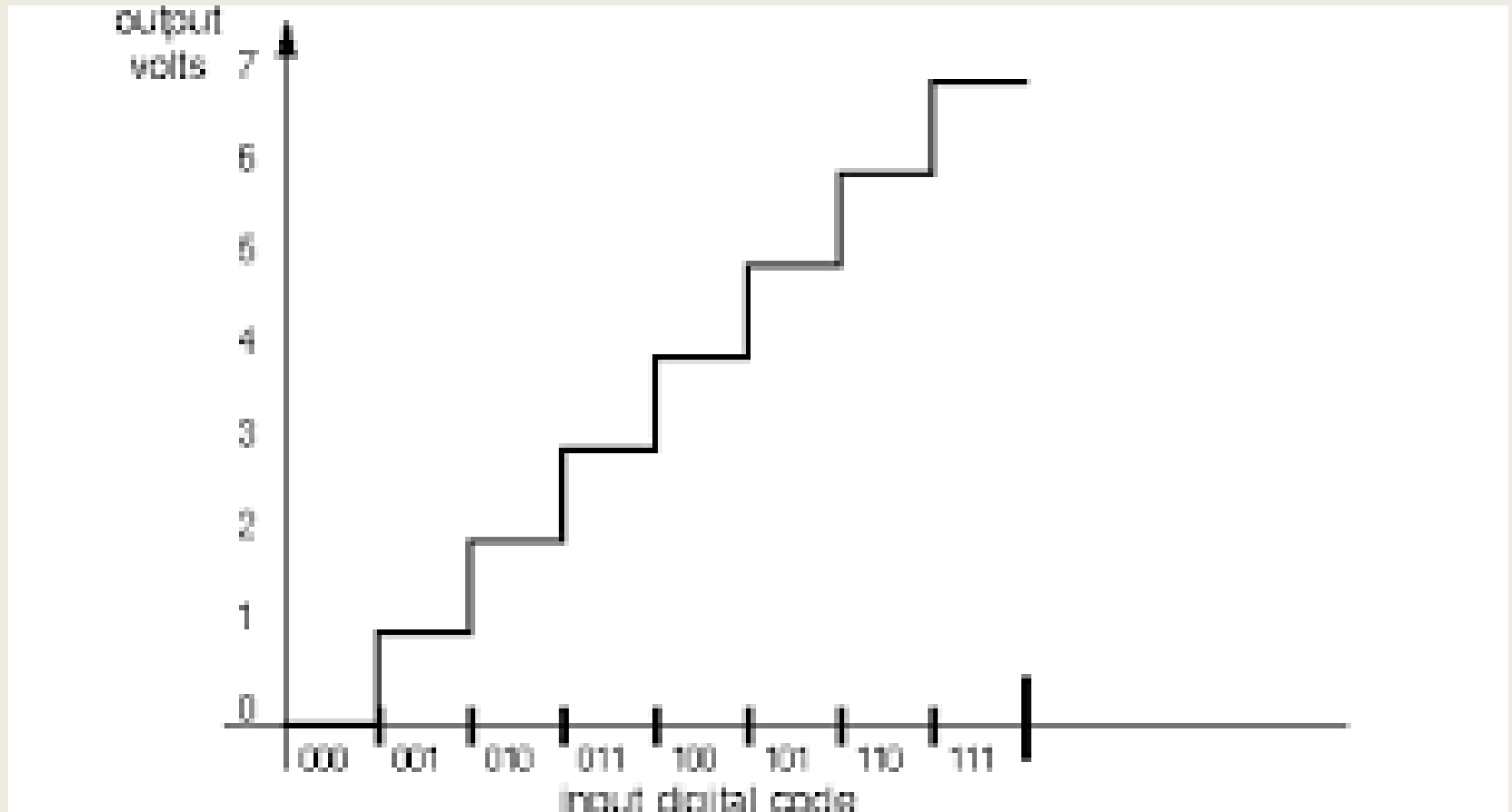
# DAC Graph

Digital input in x - axis,  
Analog Output in y - axis



# RESOLUTION

- Defined as the smallest change that can occur in the analog output when digital input changes
- resolution for DAC is in bits number  
examples  
10-bit DAC have 10 bits resolution.  
10-bit DAC has a resolution smaller than 8-bits DAC
- Resolution can be expressed in two cases, either the voltage or Ampere and also percentages.
- Resolution is usually referred to the step size since it was a total change in  $V_{out}$  when the digital input changes from one step to the next step.
- Its value is equal to the LSB wheighted

# Resolution Percentages (%)

## Formula

$$\% \text{ Resolution} = \frac{\text{Step Size}}{\text{Full Scale}} \times 100\%$$

$$\text{Full Scale} = \text{Number Of Step} \times \text{Step Size}$$

$$\text{Step Size} = \frac{\text{Full Scale}}{\text{Number Of Step}}$$

$$\% \text{ Resolusi} = \frac{1}{\text{Number Of Step}} \times 100\%$$

$$= \frac{1}{2^n - 1} \times 100\%$$

## Formula

Resolution = Step Size = Input bit for LSB

$V_{out}$  (analog output) =  $K \times$  Digital Input

$K = \frac{\text{Total Voltage/Current}}{\text{Number Of Step}}$

Or

$\frac{\text{Analog Output}}{\text{Digital Input}}$

\*  $K$  = the factor of proportionality and is a fixed value for a DAC

Digital Input = Number of Step

Number of Step =  $2^n - 1$

Where;

$n$  = Number of input bits

# ACCURACY


- Manufacturer of digital to analog converter has a several ways to define accuracy. Two of them are often referred to Linearity Error and Full-scale error

## Full Scale Error


- The maximum deviation from the ideal DAC output value.
- Examples  
4-bit DAC has  $\pm 0.01\%$ FS accuracy and DAC full-scale is 15V. So  $\pm 0.01\% \times 15 = \pm 1.5\text{mV}$ .

This means that the DAC output will be different from the ideal value 1.5mV

# BLOCK DIAGRAM

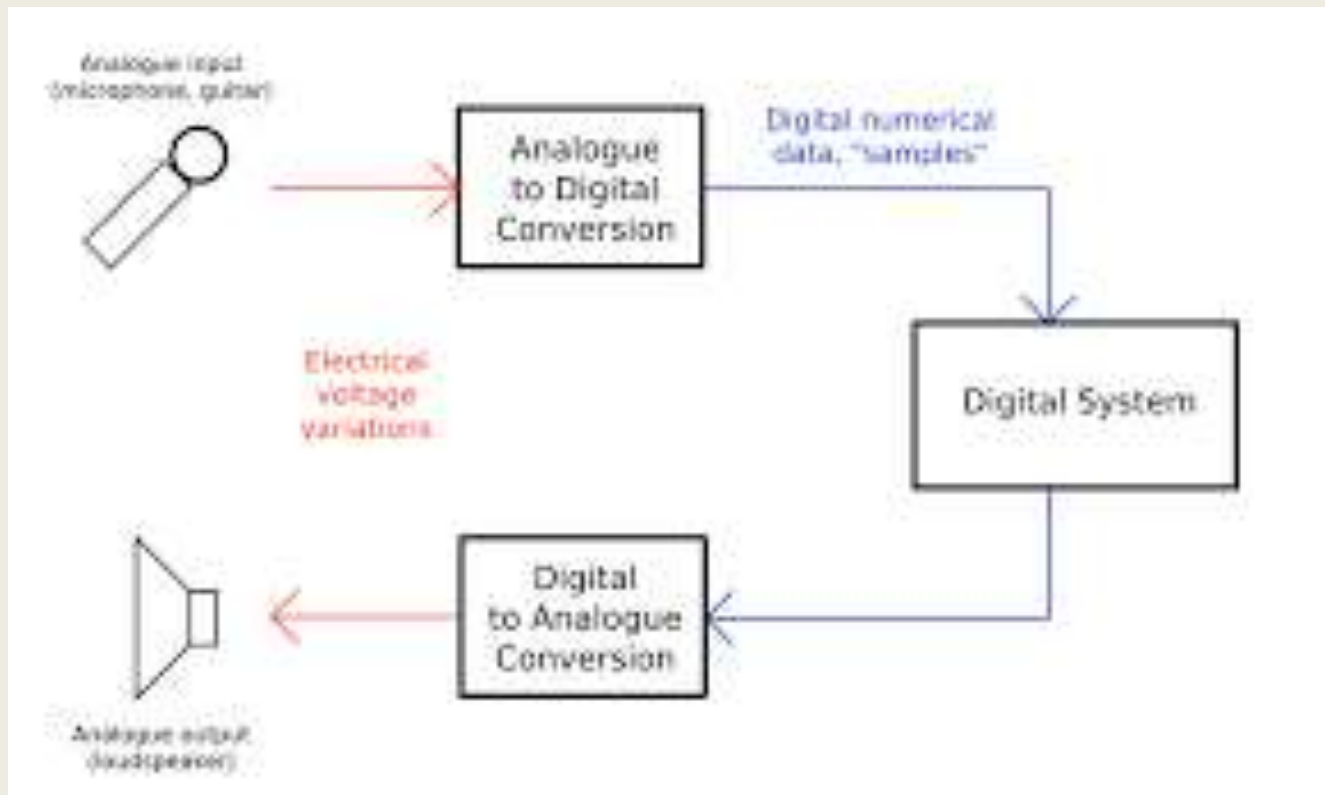

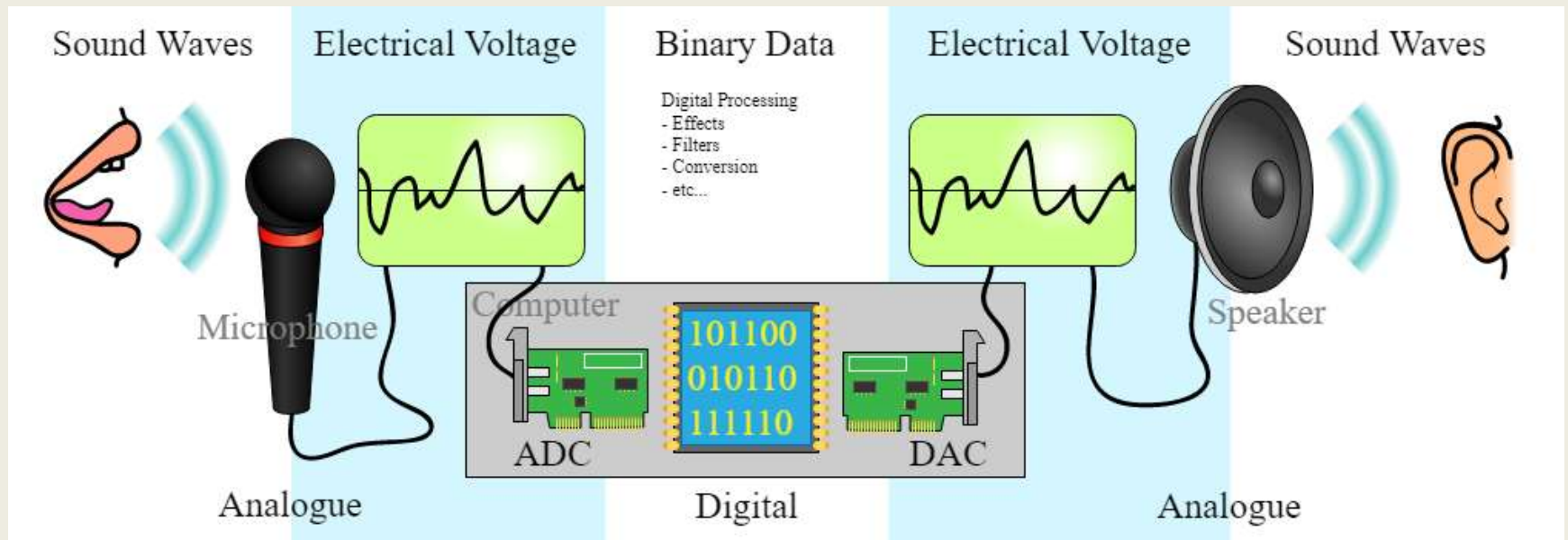
# ANALOG TO DIGITAL AND DIGITAL TO ANALOG OF SOUND SIGNAL






# SIGNAL CONVERSION

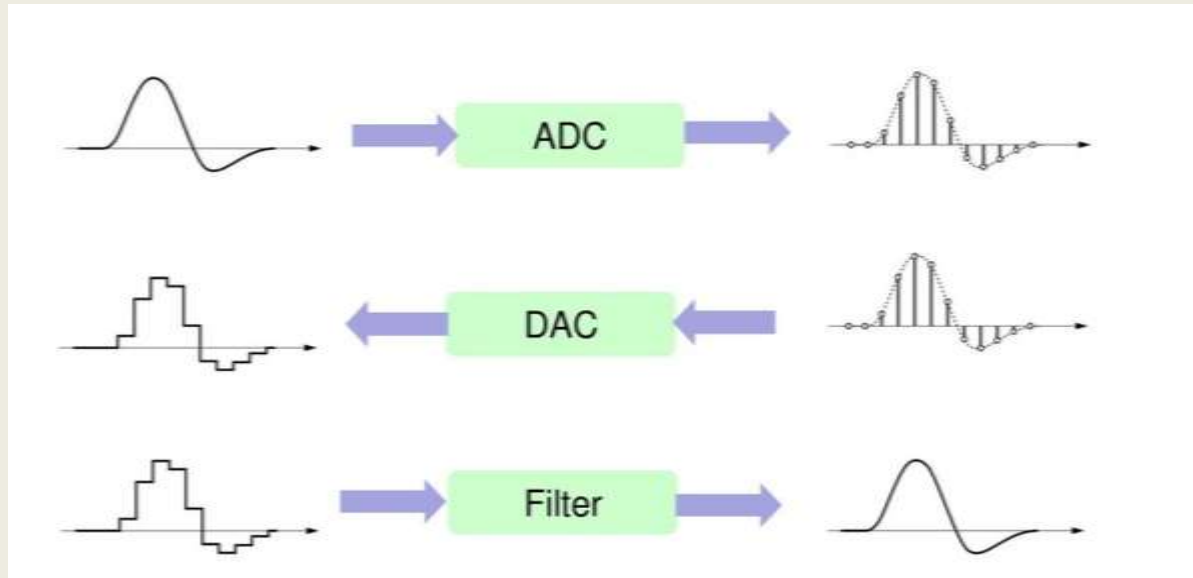

# BIT RESOLUTION

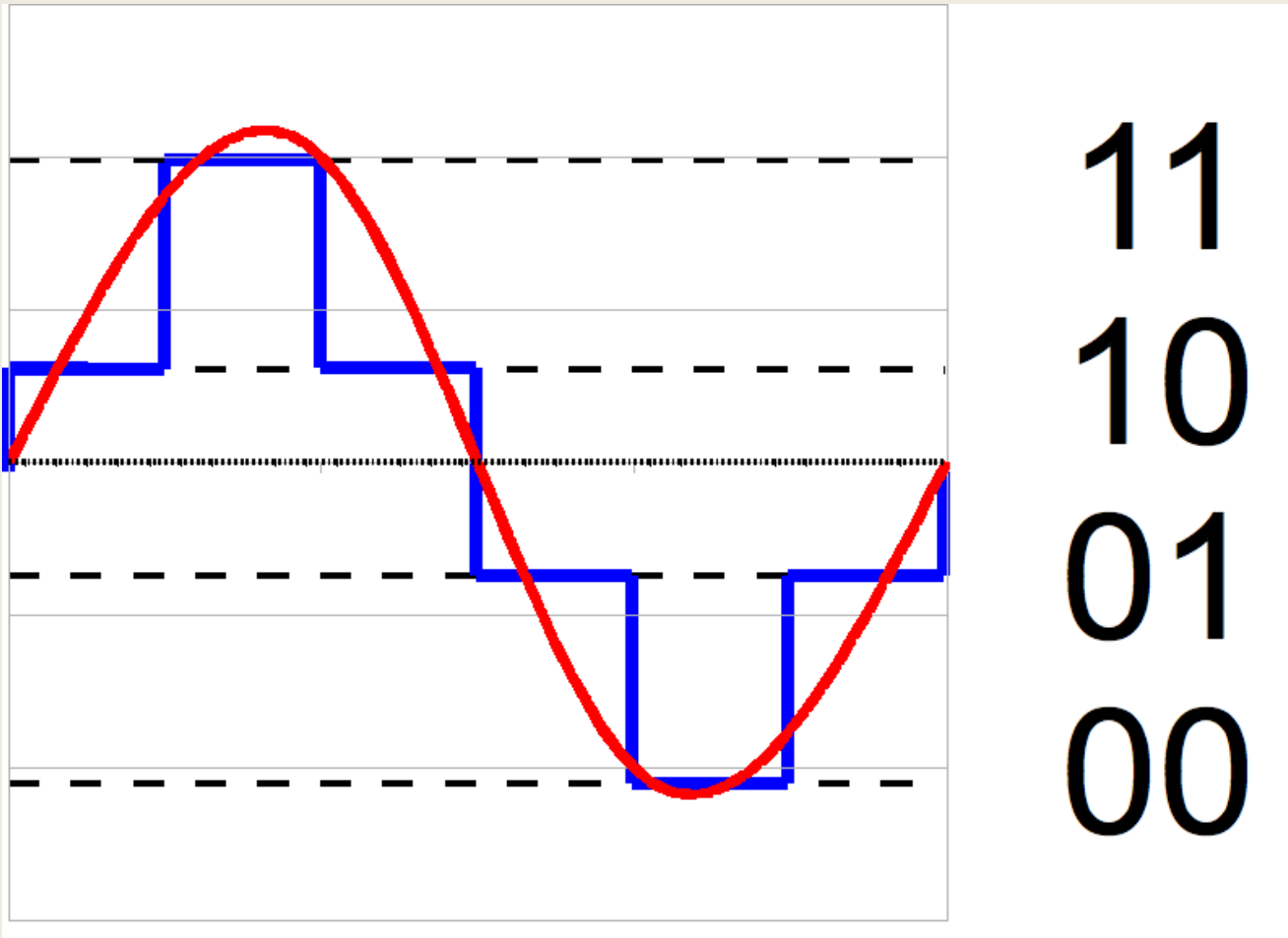

# QUESTION TIME

Students can ask questions/  
clarifications now

HAVE A NICE DAY !!!