

### 36.3 HYBRID EQUIVALENT CIRCUIT OF COMMON EMITTER AMPLIFIER

Fig. 36.7 shows the common-emitter NPN transistor amplifier circuit.  $R_g$  is the output resistance of input signal and  $R_L$  is the load resistance.

The general  $h$ -parameter expressions become,

$$V_i = V_{be} = h_{ie} I_b + h_{re} V_o \quad \dots(1)$$

$$I_c = h_{fe} I_b + h_{oe} V_o \quad \dots(2)$$

where  $V_o = V_{ce}$ .

From Eq. (1), we get

$$I_b = \frac{V_i - h_{re} V_o}{h_{ie}} \quad \dots(3)$$

The d.c. voltage of the collector with respect to the emitter is given by

$$V_{ce} = V_{cc} - I_c R_L$$

$$\therefore dV_{ce} = -R_L dI_c$$

or  $V_{ce} = -R_L i_c$

In terms of usual notations, we can write

$$V_{ce} = -R_L I_c$$

or  $V_o = -R_L I_c$

Substituting the value of  $V_o$  in Eq. (2), we have

$$I_c = h_{fe} I_b - h_{oe} R_L I_c$$

or  $h_{fe} I_b = h_{oe} R_L I_c + I_c$

$$= \frac{I_c R_L}{1/h_{oe}} + \frac{I_c R_L}{R_L} \quad \dots(4)$$

Equation (3) indicates that the base-emitter circuit is equivalent to a.c. voltage source of  $h_{re} V_o$  which opposes the a.c. input voltage  $V_i$  and is connected in series with the input resistance  $h_{ie}$ .

Equation (4) indicates that the collector-emitter circuit is equivalent to current source which supplies a current  $h_{fe} I_b$  and in parallel of which are connected the output resistance  $1/h_{oe}$  and load resistance  $R_L$ .

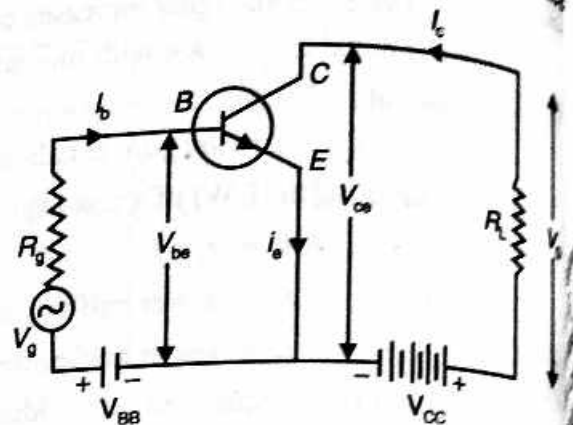


Fig. 36.7

( $\because V_{cc}$  is constant)

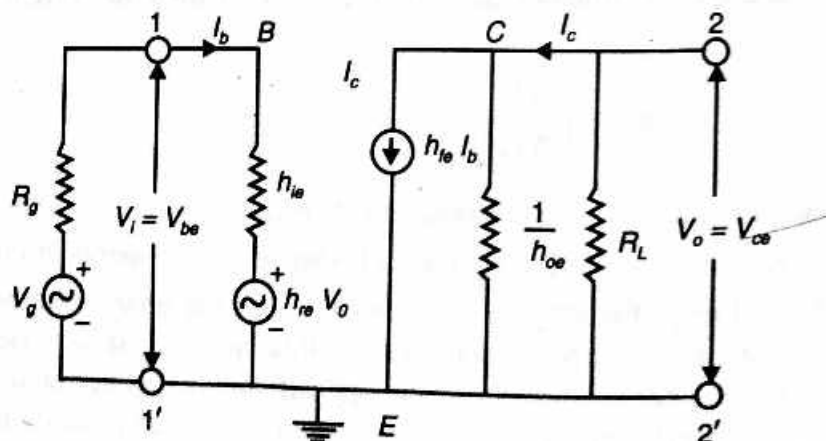


Fig. 36.8

Accordingly, the equivalent circuit is drawn in Fig. 36.8. Here the a.c. voltage source  $h_{re} V_o$  which acts in opposition to the input signal  $V_i$ , represents the 'feedback' of the output voltage to

the input circuit. The current source of magnitude  $h_{fe} I_b$  may be looked as if the input current  $I_b$  is amplified and appears as  $h_{fe} I_b$  in the output circuit. Thus  $h_{fe} = \beta$ , the current amplification factor.

### 36.3.1. Analysis of a Transistor CE Amplifier using h-parameters

Figure 36.8 shows the h-parameters equivalent circuit of a common emitter transistor amplifier. Here,

- $h_{ie}$  = input impedance,
- $h_{oe}$  = output admittance,
- $h_{fe}$  = forward current gain,
- $h_{re}$  = reverse voltage transfer ratio of the transistor.

The signal source  $V_g$  is across the input port along with its source impedance  $R_g$ . The load resistance  $R_L$  appears across the output port.  $V_i$  and  $V_o$  are the input and output signals respectively. The input and output currents are taken to be positive, while flowing inward. This circuit is an a.c. equivalent circuit and d.c. values do not appear in the circuit.  $I_b$  and  $I_c$  are the input and output currents, with the presence of the source and load.

We will now derive expressions for current gain, voltage gain, input impedance, output impedance and power gain.

(i) **Current Gain.** Let  $Z$  be the equivalent impedance of  $1/h_{oe}$  and  $R_L$  in parallel. Then,

$$\frac{1}{Z} = \frac{1}{h_{oe}} + \frac{1}{R_L} = h_{oe} + \frac{1}{R_L}$$

$$Z = \frac{R_L}{1 + h_{oe} R_L}$$

Voltage across  $R_L$  = voltage across  $Z$

$$I_c R_L = h_{fe} I_b (Z) = h_{fe} I_b \left( \frac{R_L}{1 + h_{oe} R_L} \right)$$

$$\frac{I_c}{I_b} = \frac{h_{fe}}{1 + h_{oe} R_L}$$

Current Gain  $A_{ie} = \frac{\text{Output Current}}{\text{Input Current}}$

$$A_{ie} = \frac{I_c}{I_b} = \frac{h_{fe}}{1 + h_{oe} R_L} \quad \dots(1)$$

(ii) **Input impedance.** The input impedance  $Z_{ie}$  of the transistor is the impedance at the input terminals 1 and 1'.

$$\text{Input impedance } Z_{ie} = \frac{\text{Input Voltage}}{\text{Input Current}} = \frac{V_i}{I_b}$$

But

$$V_i = h_{ie} I_b + h_{re} V_o \quad (\because V_o = -I_c R_L)$$

$$= h_{ie} I_b + h_{re} (-I_c R_L)$$

$$Z_{ie} = \frac{V_i}{I_b} = h_{ie} - h_{re} R_L \left( \frac{I_c}{I_b} \right)$$

$$Z_{ie} = h_{ie} - h_{re} R_L A_{ie} = h_{ie} - \frac{h_{re} \cdot h_{fe} \cdot R_L}{(1 + h_{oe} \cdot R_L)} \quad \dots(2)$$

(iii) Voltage gain.

$$\text{Voltage gain } A_{ve} = \frac{\text{Output Voltage } (V_0)}{\text{Input Voltage } (V_i)}$$

But

$$V_0 = -I_c R_L$$

$$A_{ve} = -\frac{I_c R_L}{V_i} = -\left(\frac{I_c}{I_b}\right)\left(\frac{I_b}{V_i}\right)R_L$$

$$= -A_{ie}\left(\frac{1}{Z_{ie}}\right)R_L = -\frac{A_{ie} R_L}{Z_i} \quad \dots(3)$$

Substituting the value of  $Z_i = Z_{ie} = h_{ie} - h_{re} R_L A_{ie}$  from Eq. (2),

$$A_{ve} = -\frac{A_{ie} R_L}{h_{ie} - h_{re} R_L A_{ie}} = \frac{R_L}{\frac{h_{ie}}{A_{ie}} - h_{re} R_L}$$

Substituting  $A_{ie} = \frac{h_{fe}}{1 + h_{0e} R_L}$  from Eq. (1), we get

$$A_{ve} = -\frac{R_L}{\frac{h_{ie}(1 + h_{0e} R_L)}{h_{fe}} - h_{re} R_L}$$

$$= -\frac{h_{fe} R_L}{h_{ie}(1 + h_{0e} R_L) - h_{fe} h_{re} R_L}$$

$$= -\frac{h_{fe} R_L}{h_{ie} + (h_{ie} h_{0e} - h_{fe} h_{re}) R_L}$$

$$= -\frac{h_{fe} R_L}{h_{ie} + R_L \Delta h} \quad \dots(4)$$

where  $\Delta h = h_{ie} h_{0e} - h_{fe} h_{re}$ .

The negative sign shows that the input and the output are 180° out of phase.

(iv) Output impedance. The output impedance  $Z_0$  of an amplifier is defined as the ratio of the output voltage to the output current with the input signal generator  $V_g$  reduced to zero and replaced by its internal resistance  $R_g$  and an a.c. voltage source  $V_0$  (rms) applied to the output terminals as shown in Fig. 36.9. Thus

$$Z_{0e} = \frac{V_0}{I_c}$$

where  $I_c$  is the current sent by the applied source.

Since the current through the output resistance  $1/h_{0e}$  is  $I_c - h_{fe} I_b$ , the output voltage  $V_0$  is given by

$$V_0 = (I_c - h_{fe} I_b) \frac{1}{h_{0e}}$$

or

$$h_{0e} V_0 = I_c - h_{fe} I_b$$

But the base current  $I_b$  is given by

$$I_b = -\frac{h_{re} V_0}{h_{ie} + R_g} \quad \dots(5)$$

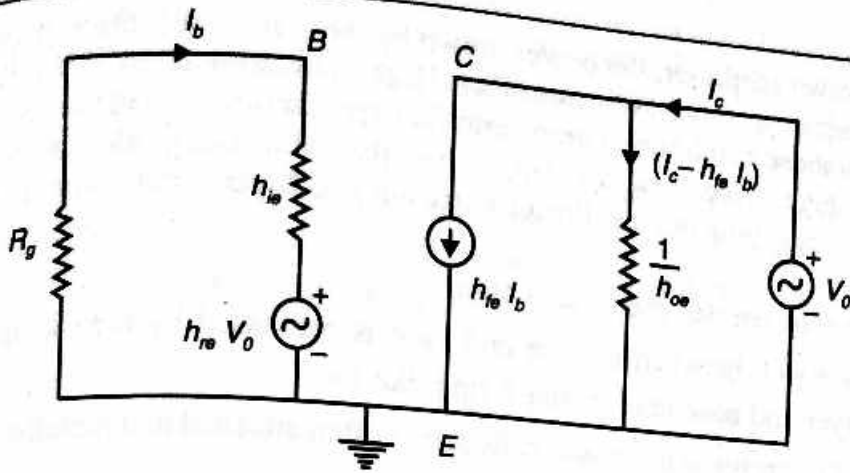


Fig. 36.9

Substituting the value of  $I_b$  in Eq. (5), we get

$$h_{0e} V_0 = I_c + \frac{h_{fe} h_{re}}{h_{ie} + R_g} V_0$$

$$V_0 \left( h_{0e} - \frac{h_{fe} h_{re}}{h_{ie} + R_g} \right) = I_c$$

$$Z_{0e} = \frac{V_0}{I_c} = \frac{1}{h_{0e} - \frac{h_{fe} h_{re}}{h_{ie} + R_g}}$$

$$Z_{0e} = \frac{h_{ie} + R_g}{h_{0e} (h_{ie} + R_g) - h_{fe} h_{re}} \quad \dots(6)$$

(v) **Power gain.** Power gain of the amplifier is the product of current gain and voltage gain.

This power gain

$$A_{pe} = |A_{ve}| \times |A_{ie}|$$

Substituting the values of  $A_{ve}$  and  $A_{ie}$  from Eqs. (4) and (1), we get

$$A_{pe} = \left( \frac{h_{fe} R_L}{h_{ie} + R_L \Delta h} \right) \left( \frac{h_{fe}}{1 + h_{0e} R_L} \right) = \frac{h_{fe}^2 R_L}{(1 + h_{0e} R_L)(h_{ie} + R_L \Delta h)} \quad \dots(7)$$

$$\Delta h = h_{ie} h_{0e} - h_{fe} h_{re}$$

In actual practice,  $h_{0e}$ ,  $h_{re}$  are very small quantities.  $h_{0e} < 1$  and  $R_L \Delta h < h_{ie}$ .

$$A_{pe} = \frac{h_{fe}^2 R_L}{h_{ie}}$$

**POWER AMPLIFIERS**

**POWER AMPLIFIER**

A transistor amplifier which raises the power level of the signals is known as power amplifier. A power amplifier actually makes a concentrated effort to obtain maximum output power. The ratio of signal power from the d.c. supply and delivers it as useful signal power to the load. The ratio of power delivered as output to the d.c. power input is known as the efficiency of the power amplifier.

In the case of power amplifier, the power drawn by the load impedance is high. This is because of high collector current in this power amplifier. High collector current is the result of low load resistances driven by these amplifiers. These amplifiers (power) are used in the last stage of cascaded amplifier. The last stage drives low resistances like that of a loudspeaker. Power amplifiers use *power transistor* as amplifying device. Power transistor is different from ordinary bipolar transistor in following aspects :

- (i) Doping level of emitter and base is high.
- (ii) Ohmic resistance between emitter and base is decreased by increasing the contact area between the base layer and base lead giving it ring like form.
- (iii) The area of collector is more and collector is often attached to a metallic heat sink in order to dissipate the generated heat.

Power amplifiers are used mainly in four modes — *class A*, *class B*, *class AB* and *class C*.

**Class A Power Amplifier.** It operates in the linear region at all times (Fig. 36.10).

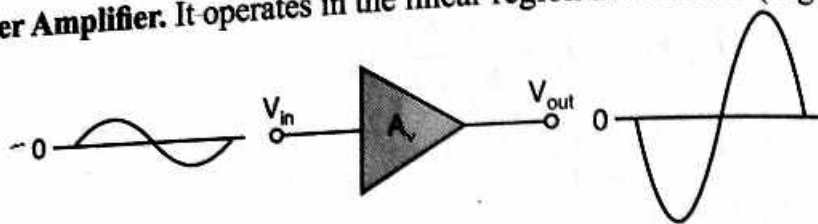


Fig. 36.10

- Output is shown  $180^\circ$  out of phase with the input (inverted).
- Class A power amplifiers are large-signal amplifiers with the objective of providing power (rather than voltage) to a load.
- In a power amplifier, it is necessary to consider the problem of heat dissipation in components.

**Power Gain.** The *power gain* of an amplifier is the ratio of the power delivered to the load to the input power.

$$A_p = \frac{P_L}{P_{in}}$$

Here,

$A_p$  = power gain

$P_L$  = signal power delivered to the load

$P_{in}$  = signal power delivered to the amplifier.

**Efficiency.** The efficiency of any amplifier is the ratio of the signal power supplied to a load to the power from the dc supply.

### 36.4.1. Class A Power Amplifier

Figure 36.11 shows a typical *class A transistor power amplifier* operating in the common emitter mode. Here resistors  $R_1$  and  $R_2$  form voltage divider circuit to provide forward biasing of the emitter-base junction.  $R_E$  is the emitter resistor for bias stabilisation and  $C_E$  is the emitter bypass capacitor which prevents the a.c. voltages from appearing across  $R_E$ . The capacitor  $C_B$  is called 'Blocking capacitor'. It is used to block d.c. component of the input signal so that only a.c. signal reaches the base. The amplifier is directly coupled to the load resistance  $R_L$ .

#### Operation of the Amplifier

The collector characteristics of the transistor used in Fig. 36.11 is shown in Fig. 36.12. The load line corresponding to  $R_L$  is drawn on the characteristics. The operating point  $Q$  is selected in almost the middle of a.c. load line.



When no signal is applied, the  $Q$ -point is operating point. When an a.c. signal is applied, the operating point shifts. It keeps on oscillating along the load line with  $Q$  as the mean position. The maximum signal condition occurs when the operation swings between saturation and cut-off.

**Efficiency:** The curves, in Fig. 36.12, show the voltage and current values at saturation and cut-off. In saturation stage, collector current is maximum and collector voltage is minimum. In cut-off stage, voltage is maximum and current is minimum. We denote voltage and current at saturation by  $V_{Cmin}$  and  $I_{Cmax}$  while these quantities at cut-off are denoted by  $V_{Cmax}$  and  $I_{Cmin}$  and at  $Q$ -point are  $V_{CQ}$  and  $I_{CQ}$ .

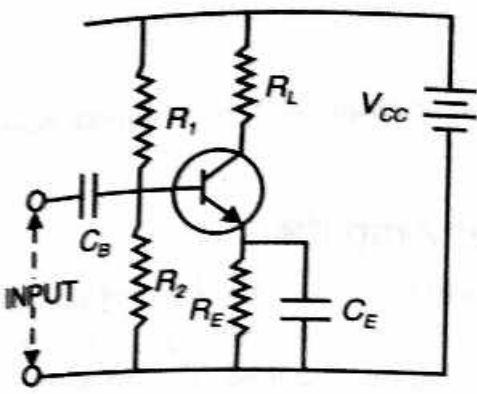


Fig. 36.11

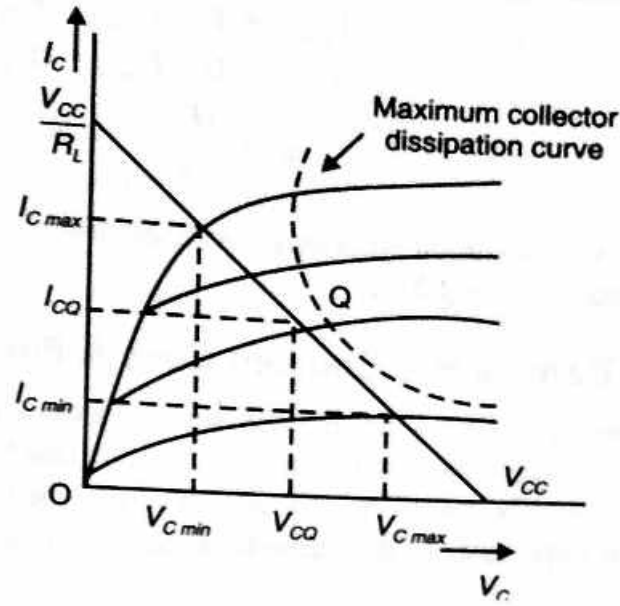


Fig. 36.12

Efficiency  $\eta$  is given by

$$\eta = \frac{\text{output a.c. power}}{\text{input d.c. power}} \quad \dots(1)$$

Input d.c. power is given by

$$P_{in} = V_{cc} I_{CQ} \quad \dots(2)$$

Output a.c. power is given by

$$P_{out} = V_{Crms} I_{Crms} \quad \dots(3)$$

Here  $V_{Crms}$  and  $I_{Crms}$  are the r.m.s. values of voltage and current. The signal makes excursions between  $V_{Cmax}$  and  $V_{Cmin}$  (or  $I_{Cmax}$  and  $I_{Cmin}$ ). So, peak values  $V_{Cm}$  and  $I_{Cm}$  of voltage and current are given by

$$V_{Cm} = \frac{V_{Cmax} - V_{Cmin}}{2}$$

$$I_{Cm} = \frac{I_{Cmax} - I_{Cmin}}{2}$$

Therefore, the a.c. output power

$$\begin{aligned} P_{out} &= V_{Crms} I_{Crms} \\ &= \frac{V_{Cm}}{\sqrt{2}} \times \frac{I_{Cm}}{\sqrt{2}} \\ &= \left( \frac{V_{Cmax} - V_{Cmin}}{2\sqrt{2}} \right) \times \left( \frac{I_{Cmax} - I_{Cmin}}{2\sqrt{2}} \right) \end{aligned}$$

$$= \frac{(V_{Cmax} - V_{Cmin})(I_{Cmax} - I_{Cmin})}{8}$$

Therefore, the efficiency of power conversion

$$\eta = \frac{P_{a.c.}}{P_{d.c.}} = \frac{(V_{Cmax} - V_{Cmin})(I_{Cmax} - I_{Cmin})}{8V_{CC} I_{CQ}}$$

For ideal collector characteristic curves

$$V_{Cmin} = 0, \quad V_{Cmax} = V_{CC}$$

$$I_{Cmin} = 0, \quad I_{Cmax} = 2I_{CQ}$$

$$\eta = \frac{(V_{CC})(2I_{CQ})}{8V_{CC} I_{CQ}} = 0.25.$$

∴ Thus the maximum efficiency obtainable from a class A amplifier when coupled directly to a load resistance is only 25%.

### 36.4.2. Transformer Coupled Class A Power Amplifier

Figure 36.13 shows the circuit diagram of a transformer coupled class A power amplifier.  $R_1$  and  $R_2$  form a potential divider arrangement to give base bias.  $V_{CC}$  provides reverse bias to the collector. The transformer is used to couple the transistor to the load. The transformer matches the output impedance of the transistor to the load resistance so that power transfer is maximum.

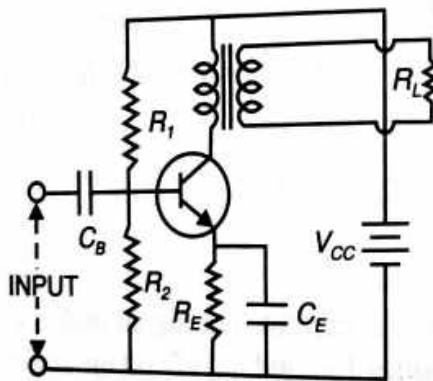


Fig. 36.13

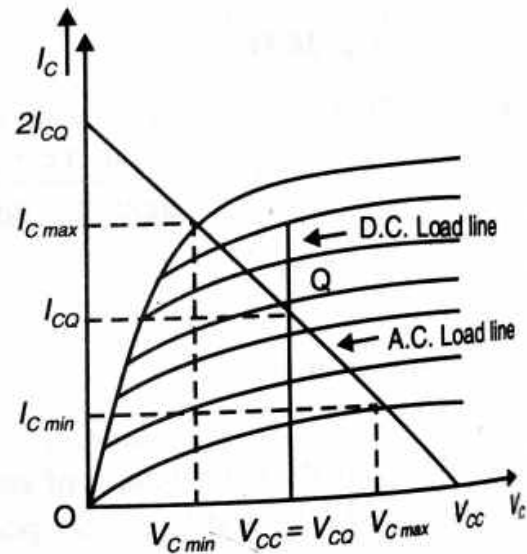


Fig. 36.14

In the circuit shown, load resistance  $R_L$  is connected across the secondary coil of the transformer. Its value as seen from the primary coil terminal is given by

$$R_L' = n^2 R_L.$$

Here,  $n$  is the turns ratio of the transformer given by

$$n = \frac{N_p}{N_s}.$$

Here  $N_p$  and  $N_s$  are the number of turns in primary and secondary coils, respectively, in power circuits. Secondary coil also has d.c. resistance, say  $R_s$ . The total resistance as seen at the primary coil terminals is given by

$$R_L' = n^2 (R_s + R_L)$$

Efficiency,

$$\eta = \frac{\text{output a.c. power}}{\text{input d.c. power}}$$

d.c. input power is given by

$$P_{in} = V_{CC} I_{CQ}$$

where  $I_{CQ}$  is the collector current at the operating point.

...(2)

Output a.c. power is given by

$$\begin{aligned} P_{out} &= V_{Crms} I_{Crms} \\ &= \frac{V_{Cm}}{\sqrt{2}} \cdot \frac{I_{Cm}}{\sqrt{2}} \\ &= \frac{(V_{Cmax} - V_{Cmin})(I_{Cmax} - I_{Cmin})}{8} \end{aligned}$$

...(3)

From Fig. 36.14, it can be seen that

$$\begin{aligned} V_{Cmax} &= 2V_{CC} & V_{Cmin} &= 0 \\ I_{Cmax} &= 2I_{CQ} & I_{Cmin} &= 0. \\ P_{out} &= \frac{4V_{CC} I_{CQ}}{8} = \frac{V_{CC} I_{CQ}}{2}. \end{aligned}$$

∴ The efficiency of power amplifier is

$$\eta = \frac{P_{a.c.}}{P_{d.c.}} = \frac{V_{CC} I_{CQ}}{2 V_{CC} I_{CQ}}$$

$$\eta = 0.5$$

∴ The efficiency of transformer coupled class A amplifier is 50% in ideal case.

### COMPARISON OF AMPLIFIER CONFIGURATIONS

The choice of configuration and the type of transistor used depends on the desired input and output impedances, current and voltage gains and the frequency response. The following table gives comparison of small signal amplifiers in the three possible configurations.

Parameter	Common base	Common emitter	Common collector
Voltage gain	High	Very-high	nearly 1
Current gain	nearly 1	high	highest
Input impedance	lowest	moderate	highest
Output impedance	highest	moderate	lowest
Phase reversal	no	yes	no

**Class B Amplifier.** Class B amplifier is biased at cutoff so that it operates in the linear region for 180° of the input cycle and is in cutoff for 180°.

Fig. 36.15 shows class B amplifier operation (noninverting).

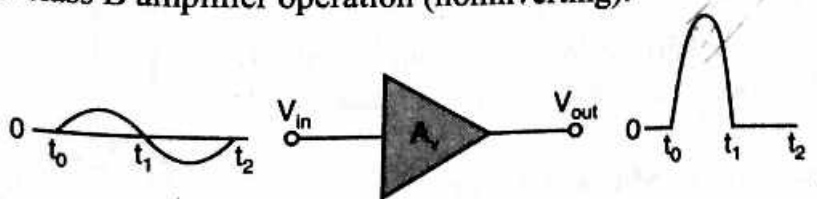


Fig. 36.15

The output waveform is shown relative to the input in terms of time ( $t$ ).  
The circuit only conducts for the positive half of the cycle.



To amplify the entire cycle, it is necessary to add a second class B amplifier that operates on the negative half of the cycle. The combination of two class B amplifiers working together is called **push-pull operation**.

We shall discuss a class B push-pull amplifier. It uses two *complementary symmetry* BJTs to reproduce the entire waveform.

### 36.5 CLASS B PUSH-PULL AMPLIFIER

Fig. 36.16 shows the circuit arrangement of a class B push-pull amplifier.

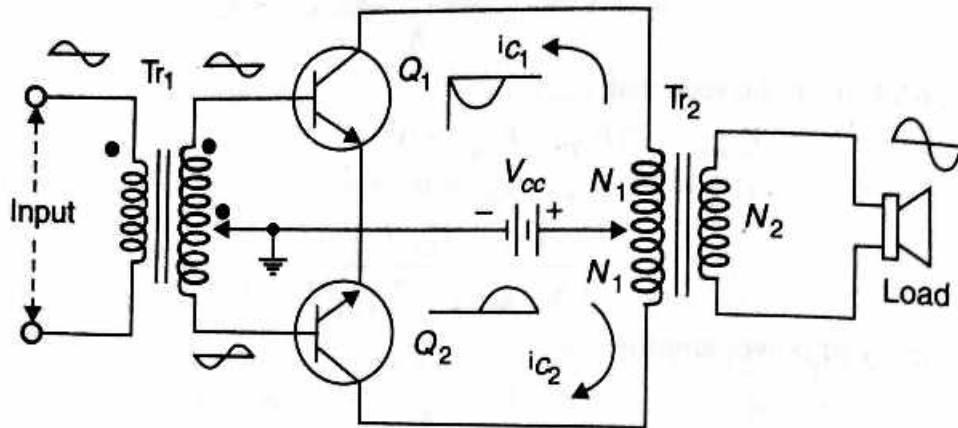


Fig. 36.16

It consists of two identical NPN transistors  $Q_1$  and  $Q_2$  placed in parallel (back to back) and operated as class B amplifiers. The input transformer  $Tr_1$  has a centre tapped secondary winding which provides opposite polarity signals to the two transistors. So the input signal drives the two transistors on alternate half cycles. The collector terminals of the transistors are connected across the primary of the output transformer  $Tr_2$ . The dc supply voltage  $V_{cc}$  is applied at the centre tap of this primary. The load resistance (loudspeaker) is connected across the secondary of the output transformer. When no signal is applied, both the transistors are cut-off.

#### Working :

(i) When the input signal is applied, the phase splitter transformer  $Tr_1$  produces two signals which are  $180^\circ$  out of phase with each other. The transistors  $Q_1$  and  $Q_2$  are driven by these two signals.

(ii) During positive half cycle of the signal, transistor  $Q_1$  conducts because its base is driven positive. Now collector current  $i_{c1}$  flows as shown in Fig. 36.16. Transistor  $Q_2$  does not conduct because its base has negative voltage. Thus  $i_{c2}$  is zero. In this way one positive half cycle of output signal appears across the primary of  $Tr_2$ .

(iii) During the negative half cycle of the input signal,  $Q_2$  is forward biased and allows a current  $i_{c2}$  to flow. Transistor  $Q_1$  becomes nonconducting.

Thus only one transistor conducts at a time.

The output transformer serves to join the two currents producing an almost undistorted output waveform as shown in Fig. 36.17.

(i) Fig. 36.17 (a) shows the input signal  $v_i$ .

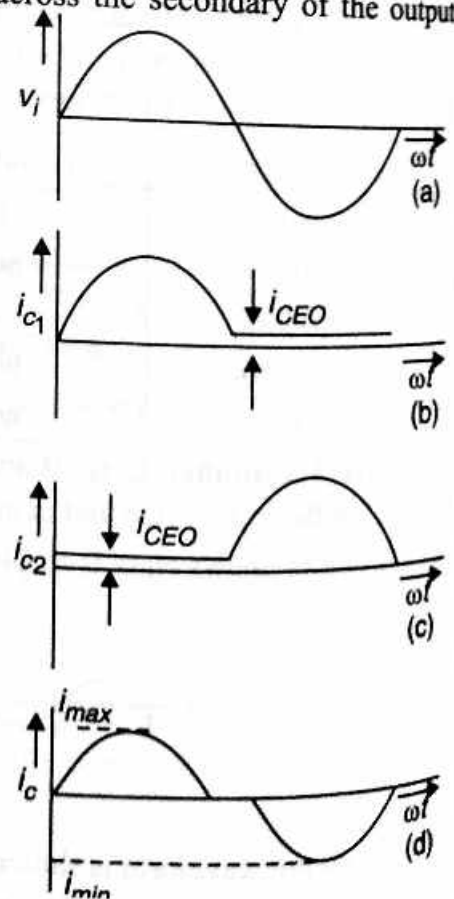


Fig. 36.17

- (ii) The collector currents in  $Q_1$  and  $Q_2$  transistors are represented by Figs. (b) and (c).
- (iii) The current responsible for output voltage across the load is represented by Fig. (d).

**Cross-Over Distortion :**

When the d.c. base voltage is zero, both transistors are off. In order that a transistor begins to conduct, the input signal voltage must have exceeded  $V_{BE}$  (Fig. 36.18). The transistor remains cut off until the base voltage exceeds 0.3 V for Ge and 0.7 V for Si.

Because of this there will be a time interval between the positive and negative alternations of the input, when neither transistor is conducting. The output does not follow the input around the zero input voltage condition. Thus the output collector current is not a uniformly enlarged sine wave at low values of current. The resulting distortion in the output waveform is called crossover distortion.

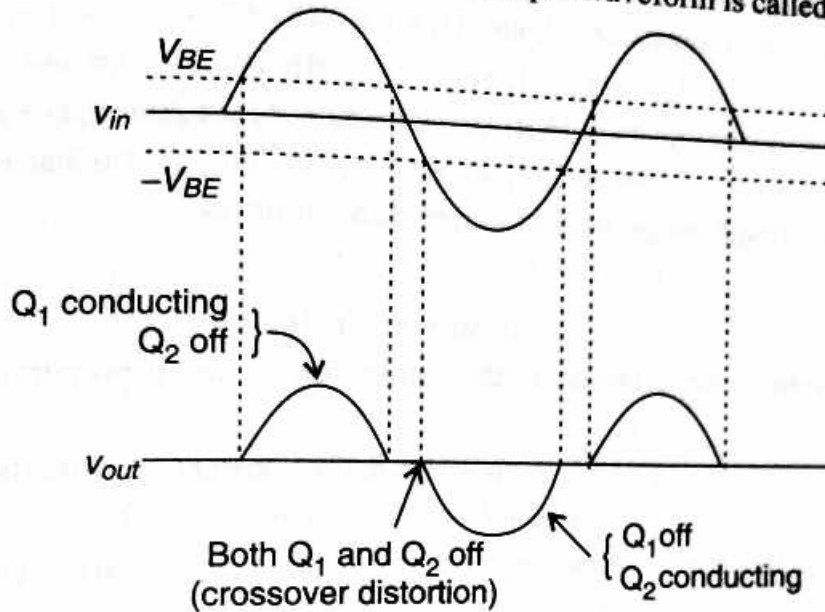


Fig. 36.18

**Power Efficiency of Class B Push-Pull Amplifier**

The current in each transistor is the average value of half sine loop.

For half sine loop,  $I_{dc}$  is given by

$$I_{dc} = \frac{(I_c)_{max}}{\pi}$$

$$(P_{in})_{dc} = 2 \times \left[ \frac{(I_c)_{max}}{\pi} \times V_{CC} \right] \quad \dots(1)$$

Here factor 2 is introduced as there are two transistors in push-pull amplifier.

R.M.S. value of collector current =  $(I_c)_{max} / \sqrt{2}$ .

R.M.S. value of output voltage =  $V_{CC} / \sqrt{2}$ .

(Under ideal conditions of maximum power)

$$(P_o)_{ac} = \frac{(I_c)_{max}}{\sqrt{2}} \times \frac{V_{CC}}{\sqrt{2}} = \frac{(I_c)_{max} \times V_{CC}}{2} \quad \dots(2)$$

Now overall maximum efficiency

$$\eta_{overall} = \frac{(P_o)_{a.c.}}{(P_{in})_{d.c.}} = \frac{(I_c)_{max} \times V_{CC}}{2} \times \frac{\pi}{2(I_c)_{max} \times V_{CC}} = \frac{\pi}{4} = 0.785 = 78.5\%$$

**Advantages.** (i) The output has much less distortion due to cancellation of even harmonics.  
 (ii) The maximum efficiency of class B push pull amplifier is quite high ( $\approx 79\%$ ).

**EXAMPLE 1.** Prove that a push-pull circuit balances all the even harmonics in the output and leaves the third harmonic term as the principal source of distortion.

(Rohilkhand, 1999, Kumaun, 2000)

**SOLUTION.** A power amplifier has to handle large signal inputs. Hence there will be harmonic distortions (frequency components in the signal getting modified) due to non-linear characteristics of the transistors used in the amplifier.

Let the input signal be sinusoidal. The base currents in the two transistors will be opposite in phase. Hence the collector currents will also be opposite in phase.

The collector currents in transistors  $Q_1$  and  $Q_2$  are given by

$$i_{c1} = A_0 + A_1 \sin \omega t + A_2 \sin 2\omega t + A_3 \sin 3\omega t + \dots \quad \dots(1)$$

and  
or

$$i_{c2} = A_0 + A_1 \sin (\omega t + \pi) + A_2 \sin 2(\omega t + \pi) + A_3 \sin 3(\omega t + \pi) \quad \dots(1)$$

$$i_{c2} = A_0 - A_1 \sin \omega t + A_2 \sin 2\omega t - A_3 \sin 3\omega t + \dots \quad \dots(2)$$

The total current through the primary of output transformer is

$$i = i_{c1} - i_{c2}$$

$$i = 2[A_1 \sin \omega t + A_3 \sin 3\omega t + \dots] \quad \dots(3)$$

The voltage induced in the secondary of the output transformer is proportional to  $i$ .

$$v_0 \propto i$$

$$v_0 = ki \quad \text{where } k \text{ is the constant of proportionality.}$$

$$v_0 = 2k[A_1 \sin \omega t + A_3 \sin 3\omega t + \dots] \quad \dots(4)$$

Thus, the output is free from even harmonics.

The principal source of distortion is the third harmonic  $3\omega$ .

## MULTISTAGE AMPLIFIERS

**Multistage Amplifiers.** Single-stage amplifiers are connected in sequence with various coupling methods to form multistage amplifiers.

- The output of one amplifier drives the input of the next.  
 The output of the first stage is used as the input to a second stage.  
 The output of the second stage is used as the input to the third stage, and so on.
- The basic purpose of a multistage arrangement is to *increase* the overall voltage gain.  
 The total voltage gain of a multistage amplifier is the *product of the individual gains* (sum of all gains).

### 36.6 MULTISTAGE VOLTAGE GAIN

Fig. 36.19 shows a multistage amplifier.

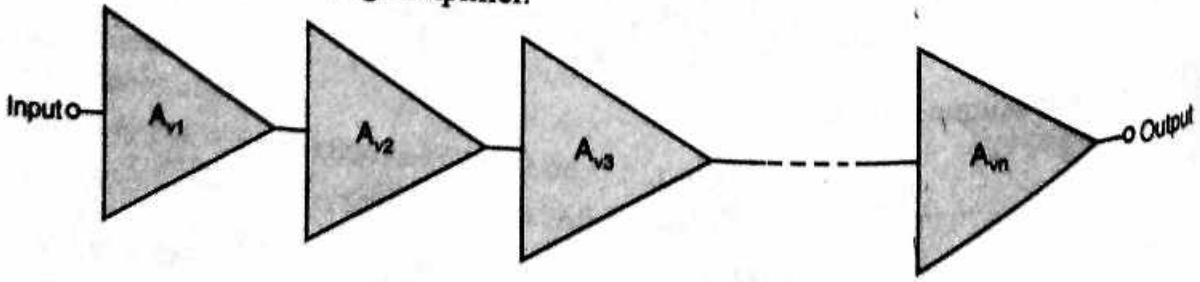


Fig. 36.19